



**K.S.RANGASAMY COLLEGE OF TECHNOLOGY, TIRUCHENGODE - 637 215**  
An Autonomous Institution, Affiliated to Anna University Chennai

EEE



**Learning by Doing - Simulation using Tinker cad**



<b>DEG / BRANCH</b>	<b>B.E( ELECTRICAL AND ELECTRONICS ENGINEERING)</b>
<b>SEMESTER</b>	<b>III</b>
<b>SUBJECT CODE</b>	<b>50 EE 302</b>
<b>SUBJECT NAME</b>	<b>ANALOG ELECTRONICS</b>
<b>Topic</b>	<b>Working of PN junction Diode</b>

**Course Instructor**  
Dr D.Sri Vidhya  
ASP / EEE

# PN JUNCTION DIODE
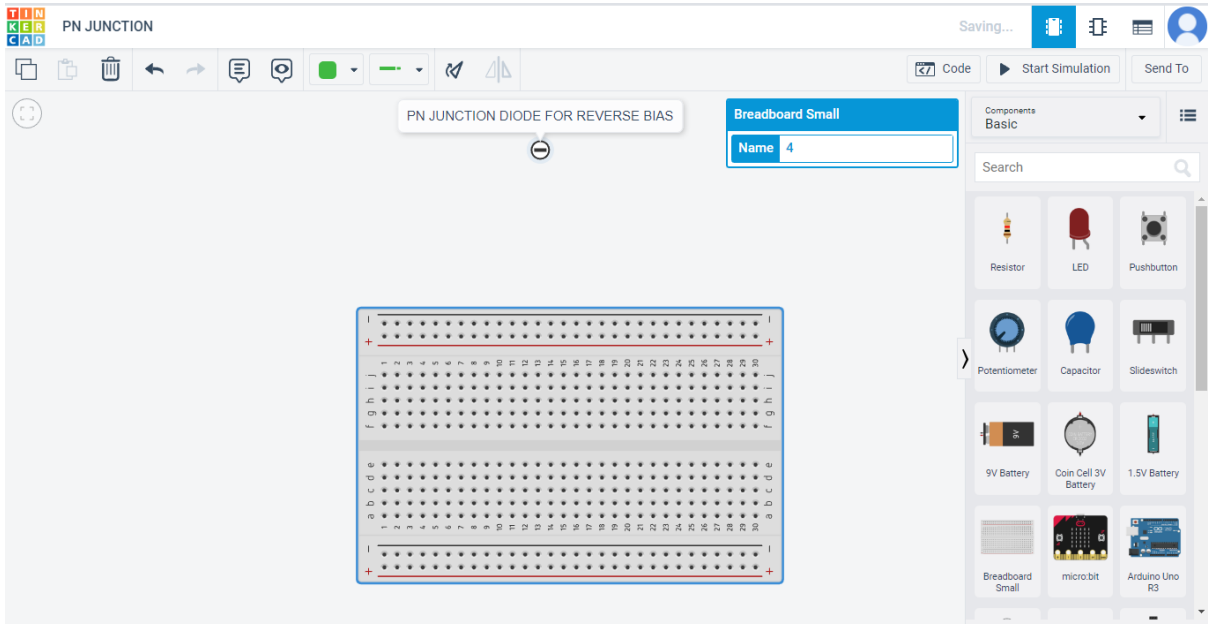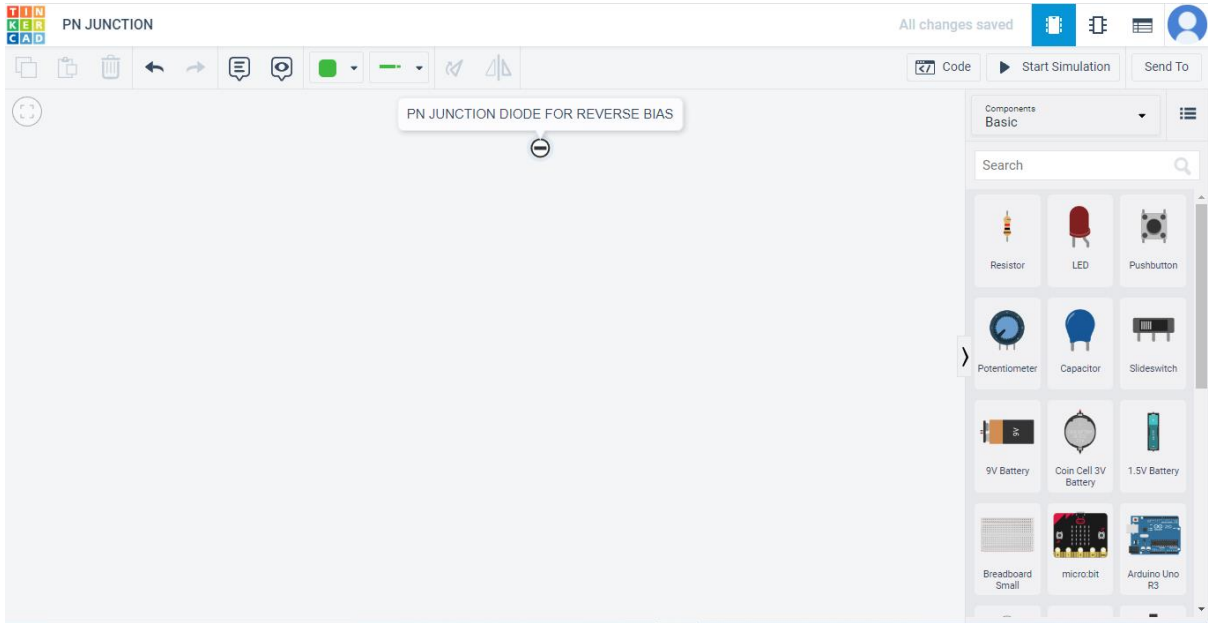
## Working of PN Junction Diode using Tinker Cad



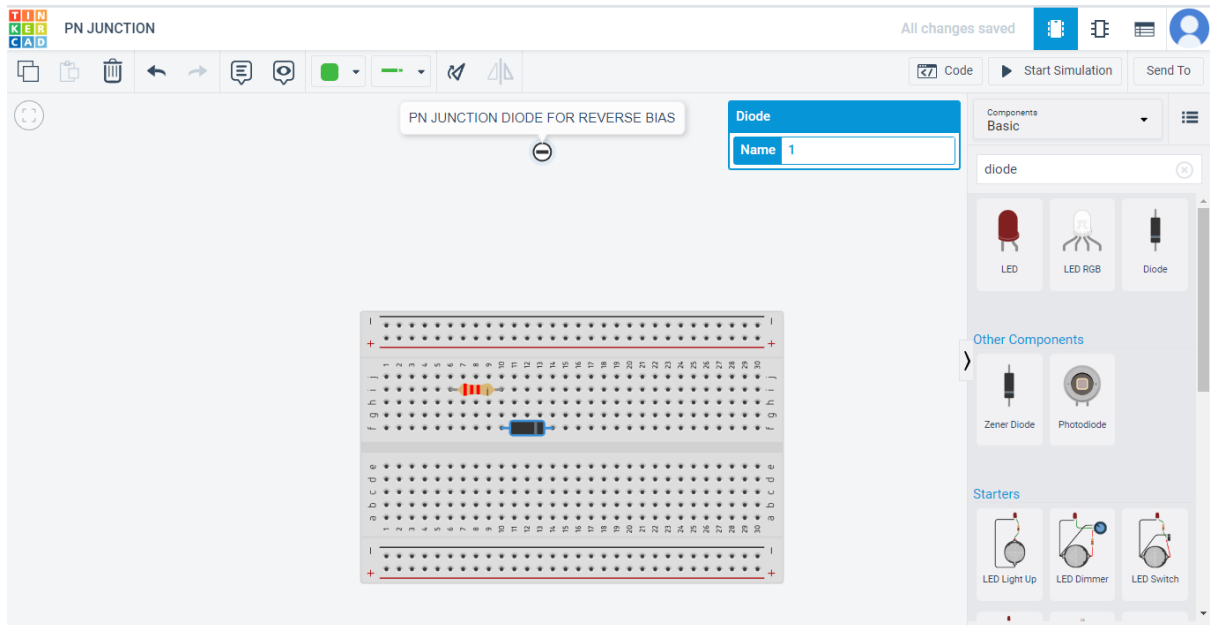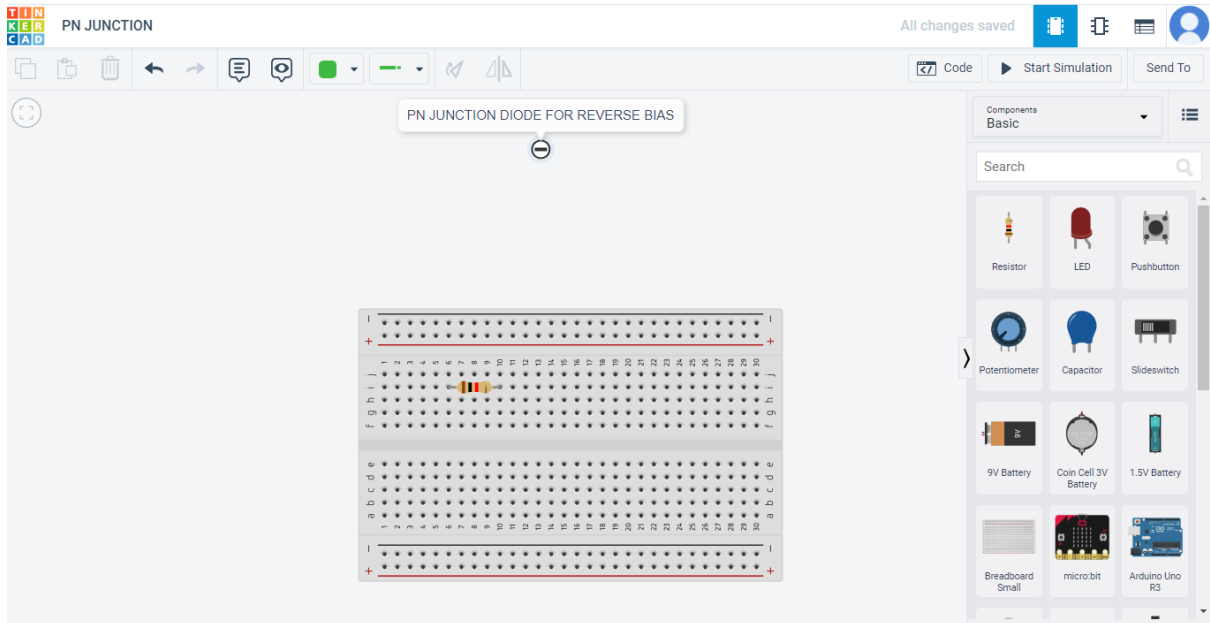

TIN KERN CAD PN JUNCTION

All changes saved

Code Start Simulation Send To

PN JUNCTION DIODE FOR REVERSE BIAS

Power Supply	
Name	1
Voltage	5
Current	5

Components Basic

power supply

Other Components

- Power Supply
- USB standard A

Starters

- Voltage Meter
- micro:bit breakout

TIN KERN CAD PN JUNCTION

All changes saved

Code Start Simulation Send To

PN JUNCTION DIODE FOR REVERSE BIAS

Multimeter	
Name	3
Mode	Voltage

Components Basic

multimeter

125.0 mA

Multimeter

